
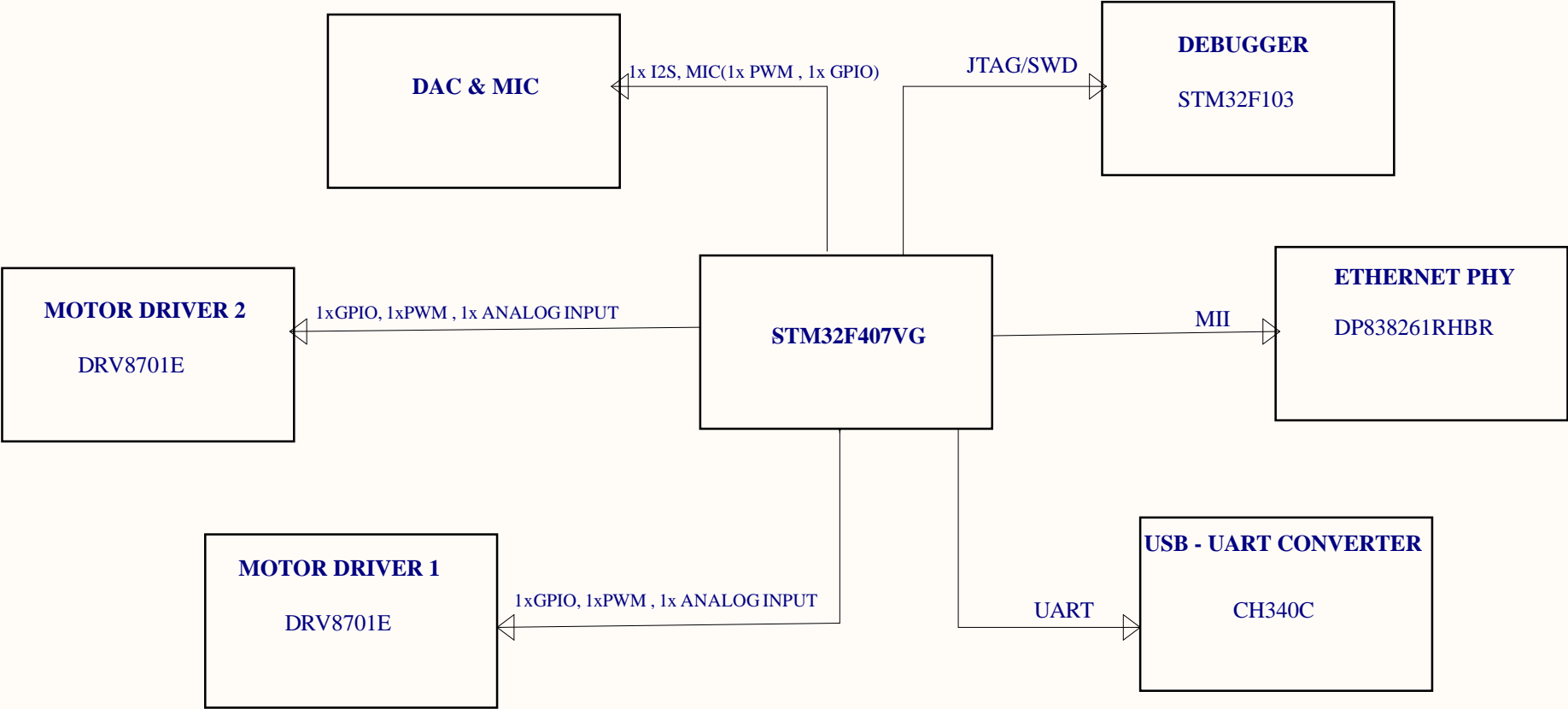



Block diagram

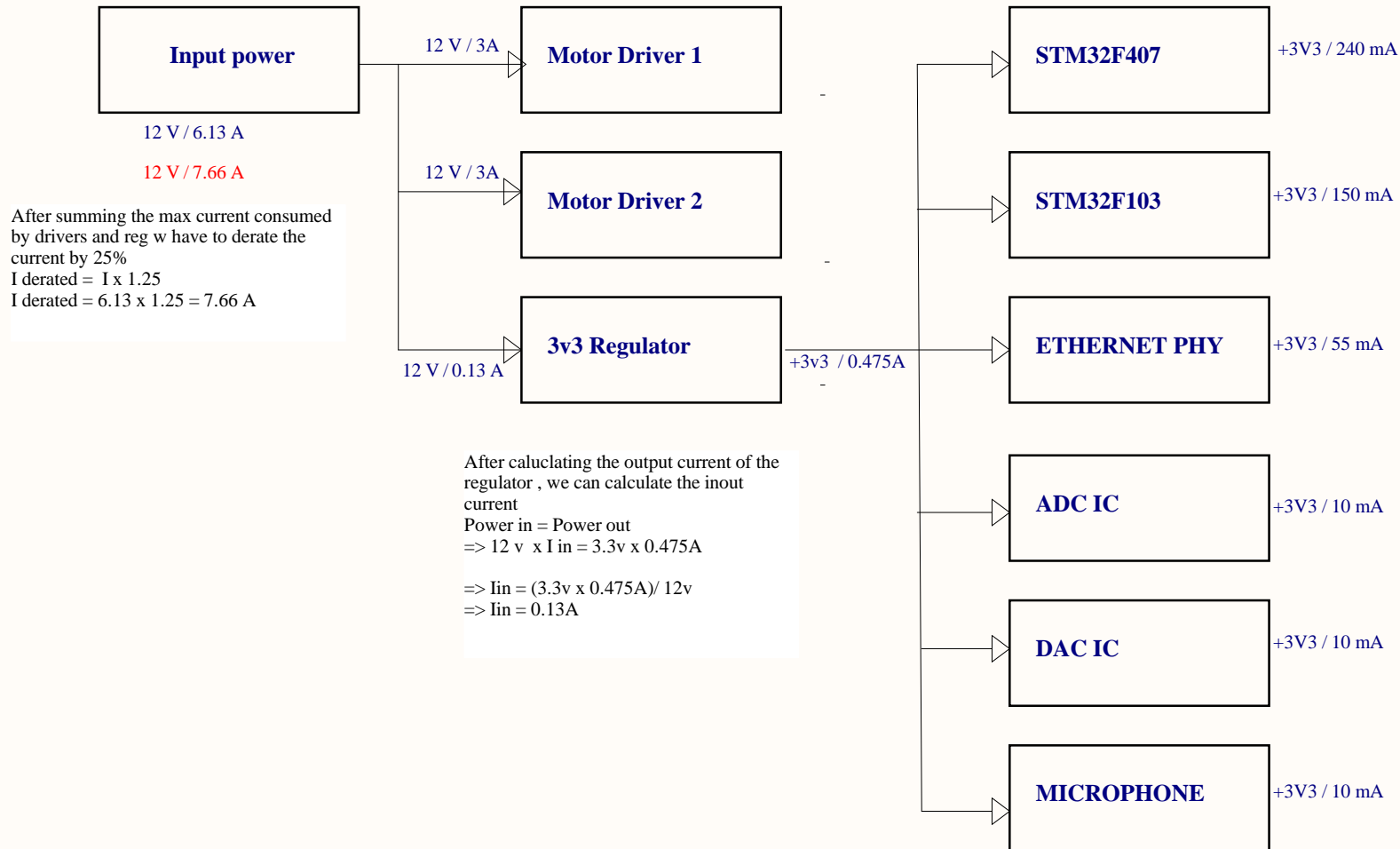


Power budget



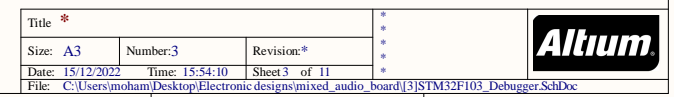First we have to get the maximum current rating of the electronics components such as stm32 and debugger ethernet phy ... then calculate the sum of currents to know how much current the regulator will supply



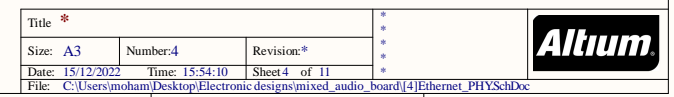

A

B

C



D


A

B


C

D

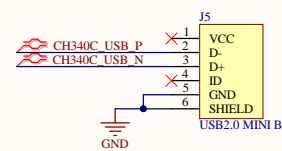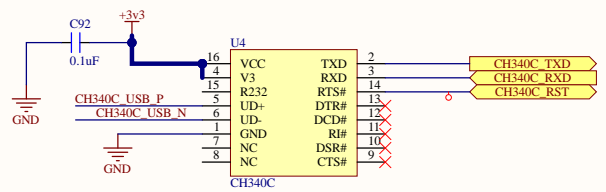

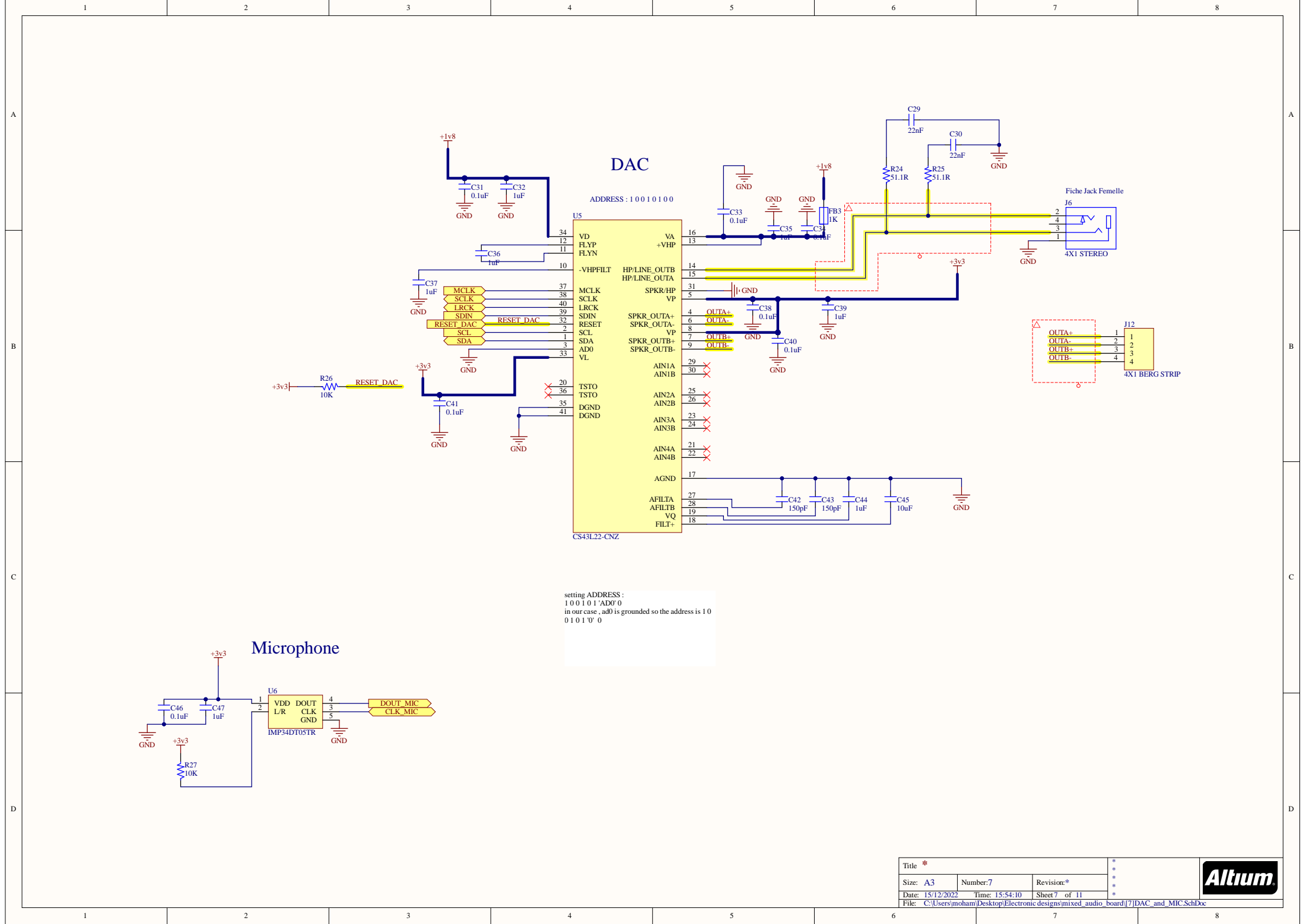

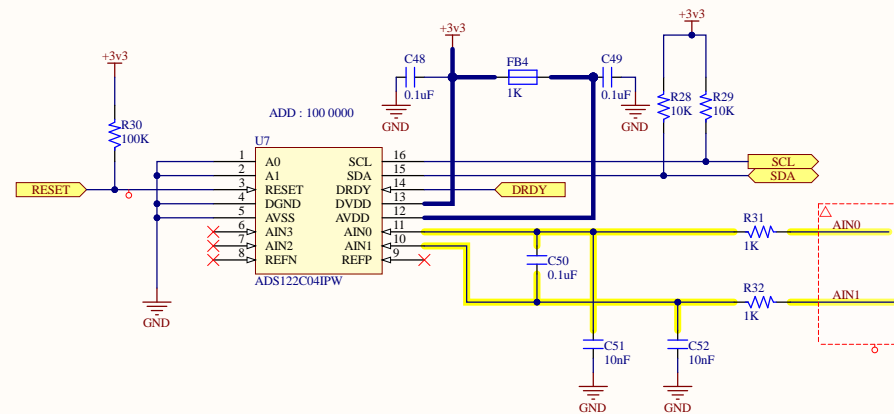setting ADDRESS :
1 0 0 1 0 1 'AD0' 0
in our case , ad0 is grounded so the address is 1 0
0 1 0 1 0' 0





I2C address

if A1 and A2 is connected to DGND I2C address is 100 0000

PULL UP resistor






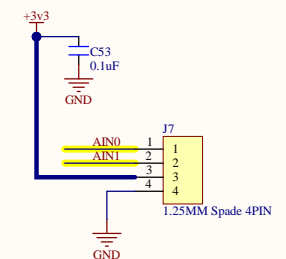
to define the value of a pull up resistor you have to see in the data sheet how much is the sink current of the pin




Title *			
Size: A3	Number: 8	Revision: *	
Date: 15/12/2022	Time: 15:54:10	Sheet 8 of 11	
File: C:\Users\moham\Desktop\Electronic designs\mixed_audio_board\8\ADC_chip.SchDoc			



MCU

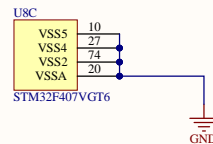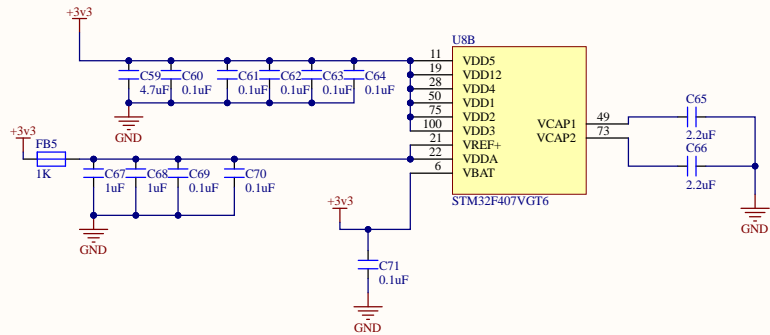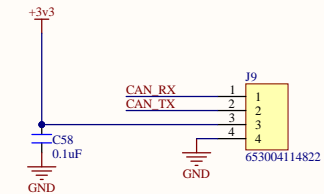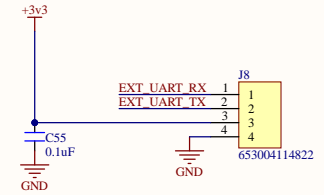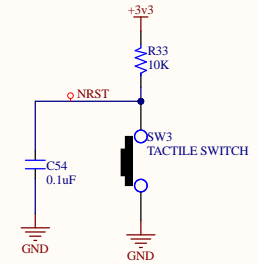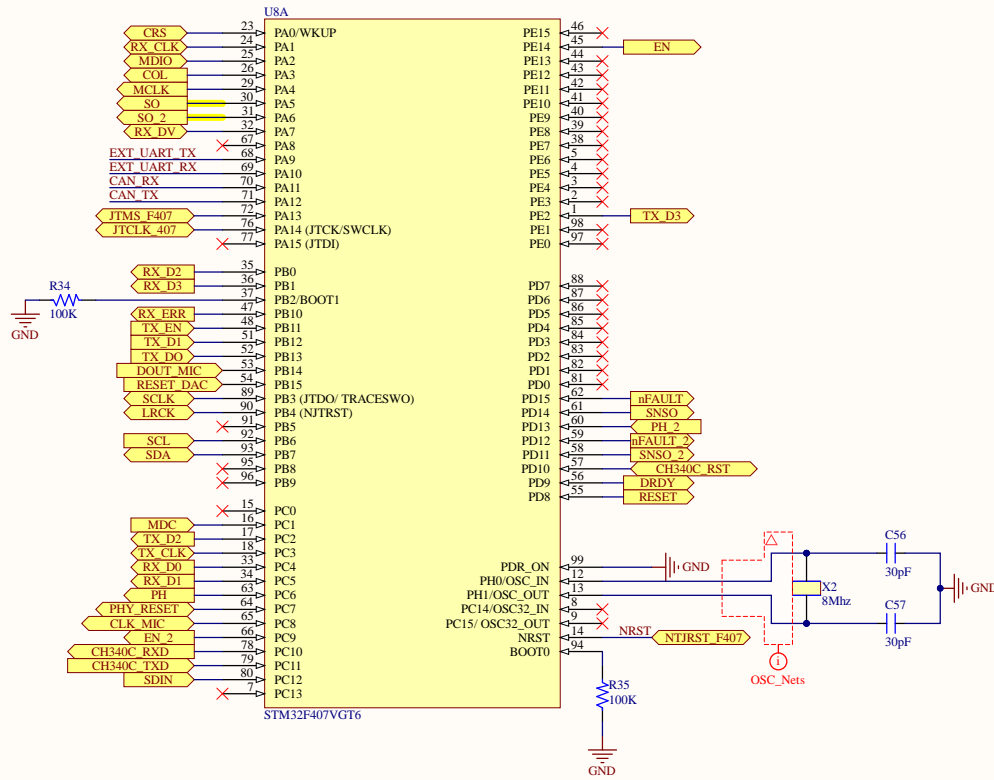

MOTOR DRIVER II

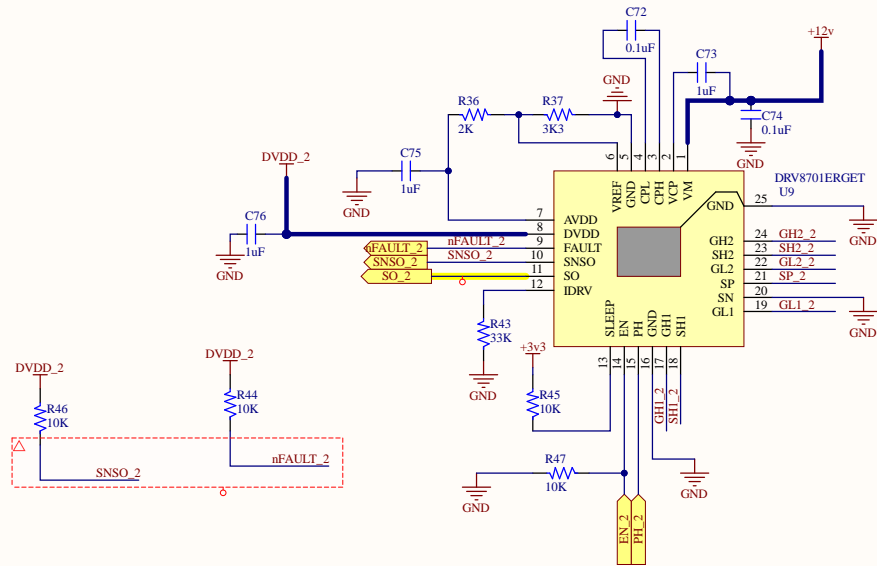

sleep pin is active low so we have to pull it high in order to make our driver works .
WE MUST connect this pin to an external 3v3 voltage and not a voltage generated by this chip otherwise it will be always off

SO is an analog signal describe the exact value of the current sensed by Rsense , we can send this signal to MCU to make a closed loop

$$I = (SO - V_{off}) / (AV \times R_{sense})$$

[datasheet]
 $V_{off} = 0.05V$
 $Av = 20$ (gain)


[calculated based on Vref and the formula on datasheet]
 $R_{sense} = (50m\Omega)$

SNSO connected to open drain this signal will be low when the current sensed exceeded the maximum current set by VRef (voltage divider) we can send this signal to our MCU to take actions based on this signal


IDRV pulled down to ground through a resistor that will assign the rise time of mosfets switching 33k is recommended by datasheet (for more details go to datasheet)

EN pin is responsible for turning the motor on and controlling its speed using pwm . we have to put pull down resistor so we prevent turning the motor on by noise

H-BRIDGE II

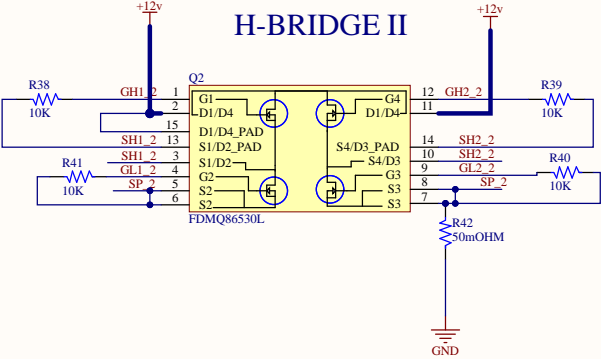

CONNECTOR II

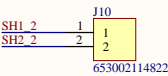

Title *			*
Size: A3			*
Number: 10			*
Revision: *			*
Date: 15/12/2022			*
Time: 15:54:10			*
Sheet 10 of 11			*
File: C:\Users\moham\Desktop\Electronic designs\mixed_audio_board\10\Motor_Driver_2.SchDoc			*



